



HACETTEPE UNIVERSITY  
COMPUTER ENGINEERING DEPARTMENT

BM233 LOGIC DESIGN LAB - 2022 FALL

---

## Assignment-1

---

December 11, 2022

*Student name:*  
Mustafa Emre  
Yıldırım

*Student Number:*  
2200356068

## 1 Problem Definition

-Four bit two's complement:

We want to inverse the 4 bit binaries.

Four bit 2x1 mux:

We want to choose one of the 2 given 4 bit binaries.

Four bit rca:

We want to add 2 given 4 bit binaries.

Four bit adder subtractor:

We want to select between add and subtract operation, if add is selected we add 2 given 4 bit binaries else we subtract them.

## 2 Solution Implementation

### 1- Two's Complement

```
module two_s_complement(In,Out);
    input [3:0] In;
    output [3:0] Out;

    assign Out[0] = In[0];
    assign Out[1] = In[1] ^ In[0];
    assign Out[2] = In[2] ^ (In[1] | In[0]);
    assign Out[3] = In[3] ^ (In[2] | In[1] | In[0]);

endmodule
```

### 2-Four Bit 2x1 Mux

```
module four_bit_2x1_mux(In_1, In_0, Select, Out);
    input [3:0] In_1;
    input [3:0] In_0;
    input Select;
    output [3:0] Out;

    assign Out = (Select) ? In_1 : In_0;
endmodule
```

---

### 3-Four Bit Rca

```
module four_bit_rca(  
    input [3:0] A,  
    input [3:0] B,  
    input Cin,  
    output [3:0] S,  
    output Cout  
);  
    wire c1;  
    wire c2;  
    wire c3;  
    full_adder fa0(.A(A[0]), .B(B[0]), .Cin(Cin), .S(S[0]), .Cout(c1));  
    full_adder fa1(.A(A[1]), .B(B[1]), .Cin(c1), .S(S[1]), .Cout(c2));  
    full_adder fa2(.A(A[2]), .B(B[2]), .Cin(c2), .S(S[2]), .Cout(c3));  
    full_adder fa3(.A(A[3]), .B(B[3]), .Cin(c3), .S(S[3]), .Cout(Cout));  
  
endmodule
```

### 4-Four Bit Adder Subtractor

```
module four_bit_adder_subtractor(A, B, subtract, Result, Cout);  
    input [3:0] A;  
    input [3:0] B;  
    input subtract;  
    output [3:0] Result;  
    output Cout;  
  
    wire [3:0] complementB,selectedBit;  
    two_s_complement f1(B,complementB);  
    four_bit_2x1_mux f2(complementB, B, subtract, selectedBit);  
    four_bit_rca f3(A,selectedBit,0,Result,Cout);  
endmodule
```

### 3 TestBench Implementation

#### 1- Two's Complement

```
`timescale 1ns/10ps
module two_s_complement_tb;

    reg [3:0] In;
    wire [3:0] Out;
    two_s_complement UUT(In,Out);
)
    initial begin
        In[0]=0; In[1]=0; In[2]=0; In[3]=0;
        In[0]=0; In[1]=0; In[2]=0; In[3]=1; #10;
        In[0]=0; In[1]=0; In[2]=1; In[3]=0; #10;
        In[0]=0; In[1]=0; In[2]=1; In[3]=1; #10;
        In[0]=0; In[1]=1; In[2]=0; In[3]=0; #10;
        In[0]=0; In[1]=1; In[2]=0; In[3]=1; #10;
        In[0]=0; In[1]=1; In[2]=1; In[3]=0; #10;
        In[0]=0; In[1]=1; In[2]=1; In[3]=1; #10;
        In[0]=1; In[1]=0; In[2]=0; In[3]=0; #10;
        In[0]=1; In[1]=0; In[2]=0; In[3]=1; #10;
        In[0]=1; In[1]=0; In[2]=1; In[3]=0; #10;
        In[0]=1; In[1]=0; In[2]=1; In[3]=1; #10;
        In[0]=1; In[1]=1; In[2]=0; In[3]=0; #10;
        In[0]=1; In[1]=1; In[2]=0; In[3]=1; #10;
        In[0]=1; In[1]=1; In[2]=1; In[3]=0; #10;
        In[0]=1; In[1]=1; In[2]=1; In[3]=1; #10;
    )
    end
endmodule
```

#### 2-Four Bit 2x1 Mux

```
`timescale 1ns/10ps
module four_bit_2x1_mux_tb;
    reg [3:0] In0,In1;
    reg Select;
    wire [3:0] Out;
    four_bit_2x1_mux UUT(In1, In0, Select, Out);
    integer i,k,s;
    initial begin
        for(i=4'b0000;i<4'b1111;i=i+4'b0001)begin
            for(k=4'b0000;k<4'b1111;k=k+4'b0001)begin
                for(s=0;s<2;s=s+1)begin
                    In0=i;In1=k;Select=s;
                    #10;
                end
            end
        end
    end
endmodule
```

### 3-Four Bit Rca

```
`timescale 1 ns/10 ps
module four_bit_rca_tb;
    reg [3:0] A;
    reg [3:0] B;
    reg Cin;
    wire [3:0] S;
    wire Cout;
    four_bit_rca UUT(.A(A), .B(B), .Cin(Cin), .S(S), .Cout(Cout));
    integer i,k,s;
    initial begin
        for(i=4'b0000;i<4'b1111;i=i+4'b0001)begin
            for(k=4'b0000;k<4'b1111;k=k+4'b0001)begin
                for(s=1'b0;s<=1'b1;s=s+1'b1)begin
                    A=i;B=k;Cin=s;
                    #10;
                end
            end
        end
    end
endmodule
```

### 4-Four Bit Adder Subtractor

```
`timescale 1ns/1ps
module four_bit_adder_subtractor_tb;
    reg [3:0] A,B;
    reg Subtract;
    wire [3:0] Out;
    wire Cout;
    four_bit_adder_subtractor UUT(A, B, Subtract, Out,Cout);
    integer i,k,s;
    initial begin
        for(i=4'b0000;i<4'b1111;i=i+4'b0001)begin
            for(k=4'b0000;k<4'b1111;k=k+4'b0001)begin
                for(s=0;s<2;s=s+1)begin
                    A=i;B=k;Subtract=s;
                    #10;
                end
            end
        end
    end
endmodule
```

## 4 Results

### 1-Two's Complement


I used k-mapping method for two's complement's derive equations

Out[0] formula:  $F(\text{In}[3], \text{In}[2], \text{In}[1], \text{In}[0]) = P(1, 3, 5, 7, 9, 11, 13, 15)$

Out[1] formula:  $F(\text{In}[3], \text{In}[2], \text{In}[1], \text{In}[0]) = P(1, 2, 5, 6, 9, 10, 13, 14)$


Out[2] formula:  $F(\text{In}[3], \text{In}[2], \text{In}[1], \text{In}[0]) = P(1, 2, 3, 4, 9, 10, 11, 12)$

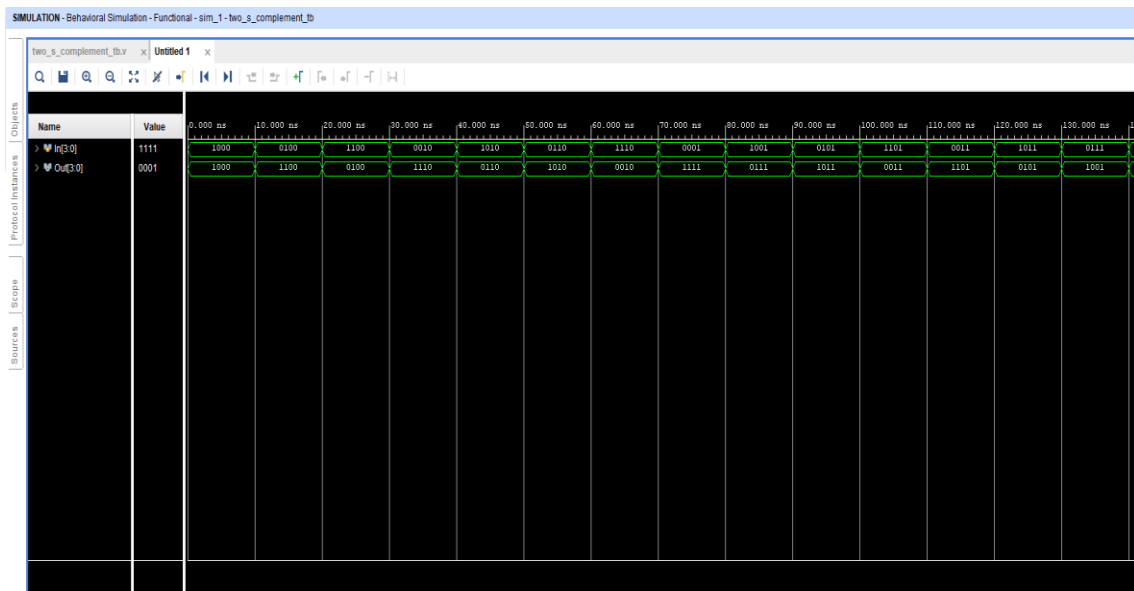Out[3] formula:  $F(\text{In}[3], \text{In}[2], \text{In}[1], \text{In}[0]) = P(1, 2, 3, 4, 5, 6, 7, 8, 10)$



 
## 2-Four Bit 2x1 Mux:

I used this link <http://www.asic-world.com/examples/verilog/mux.html> for 2x1 Mux



## 3-Four Bit Rca

I used 4 Full Adder for Four Bit Rca

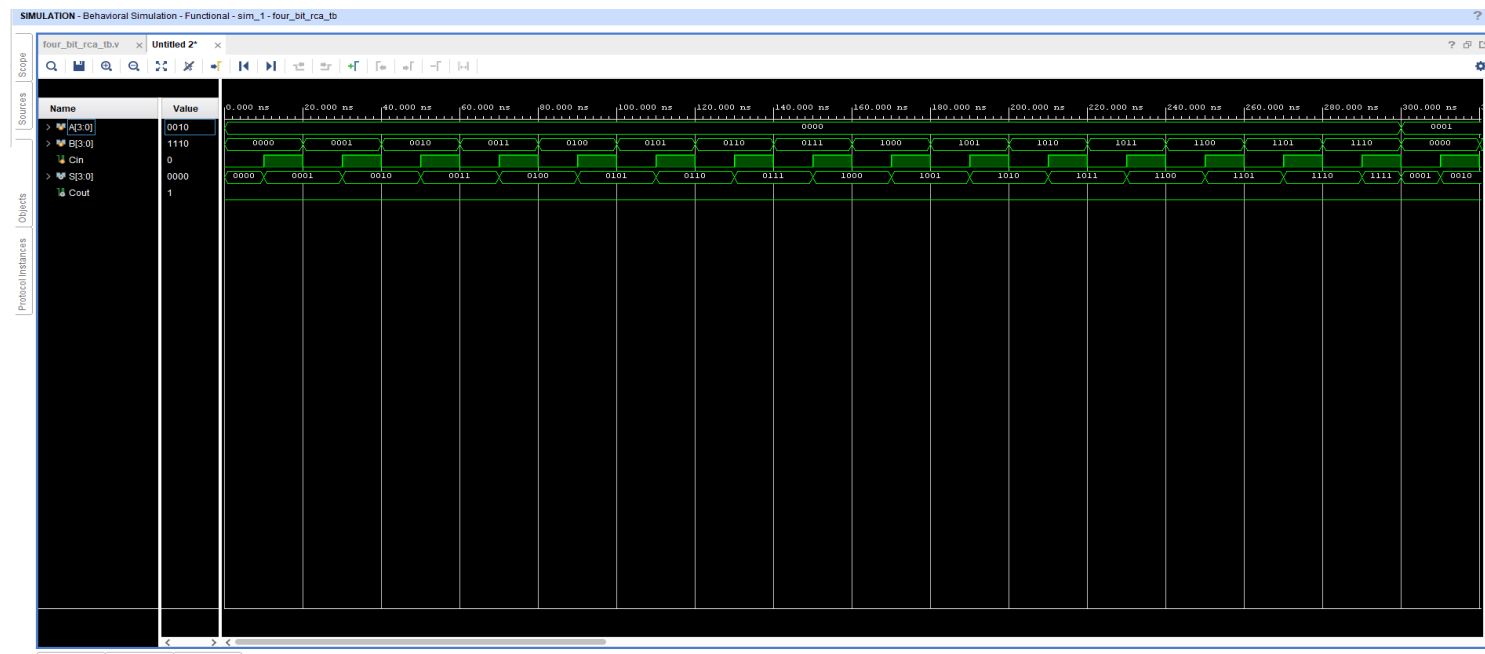

## 4-Four Bit Adder Subtractor:

I used two's complement , four bit 2x1 mux and fou

